

Gillian Kearney

Lab Report

ECE 2031 L01

27 January 27, 2022

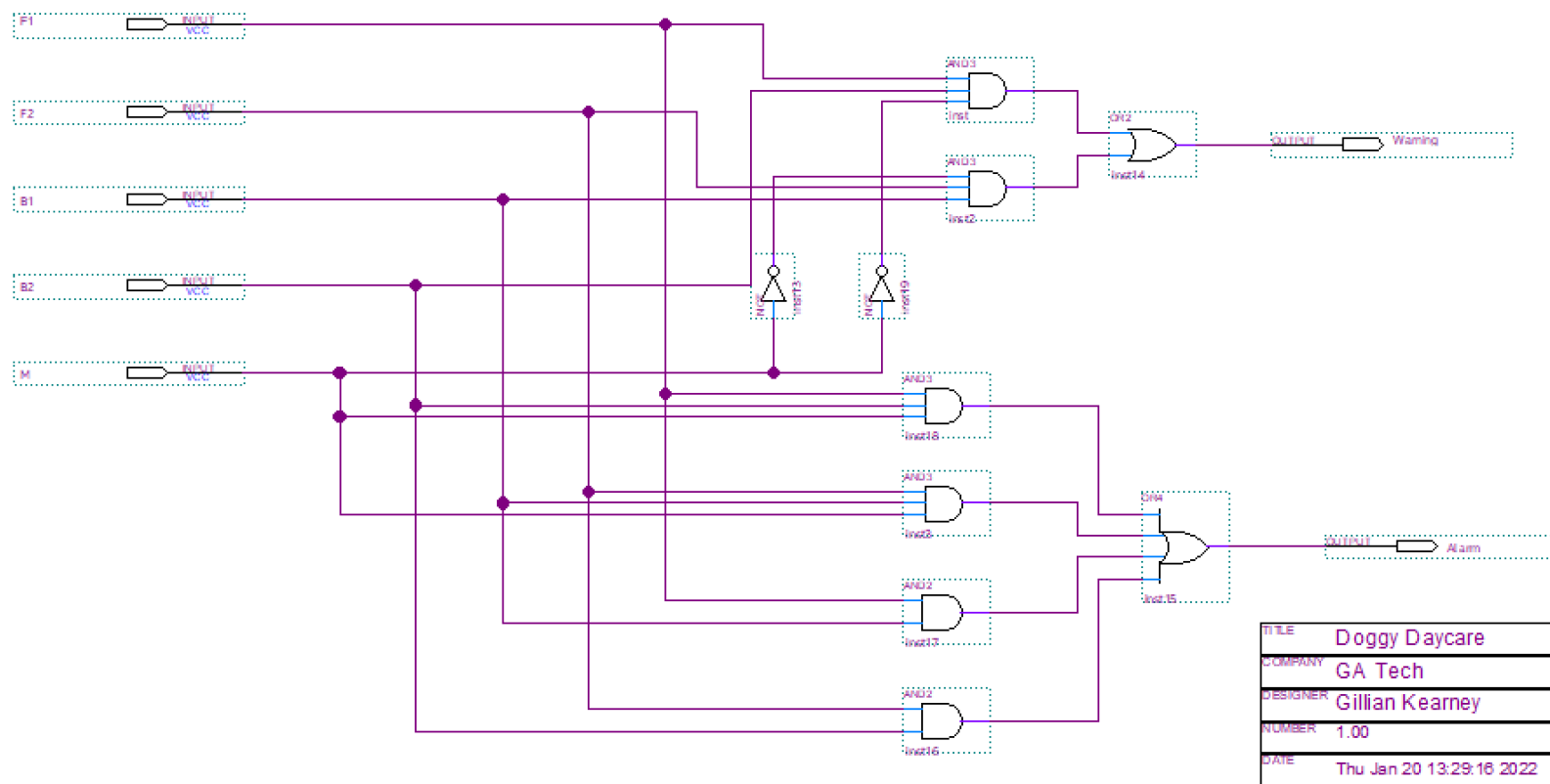


Figure 1. Circuit that activates an alarm and warning. The alarm output follows the following logic: $\text{Alarm} = F1 \cdot B1 + F2 \cdot B2 + F2 \cdot B2 \cdot M + F2 \cdot B1 \cdot M$. The warning follows: $\text{Warning} = F1 \cdot B2 \cdot /M + F2 \cdot B1/M$.

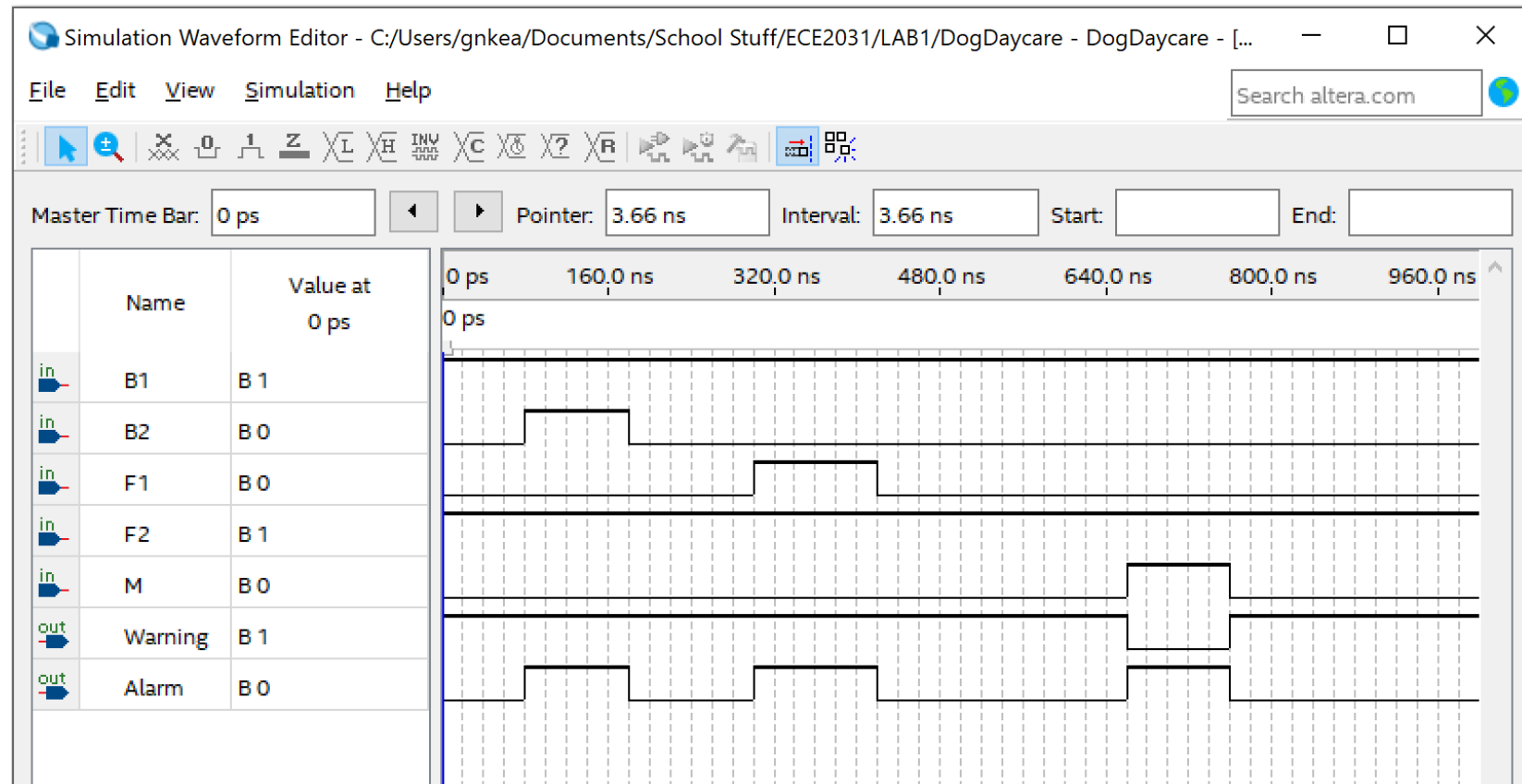


Figure 2. Functional simulation waveform implementing the dog alarm/warning system for a subset of all possible input combinations to determine the accuracy of the circuit.

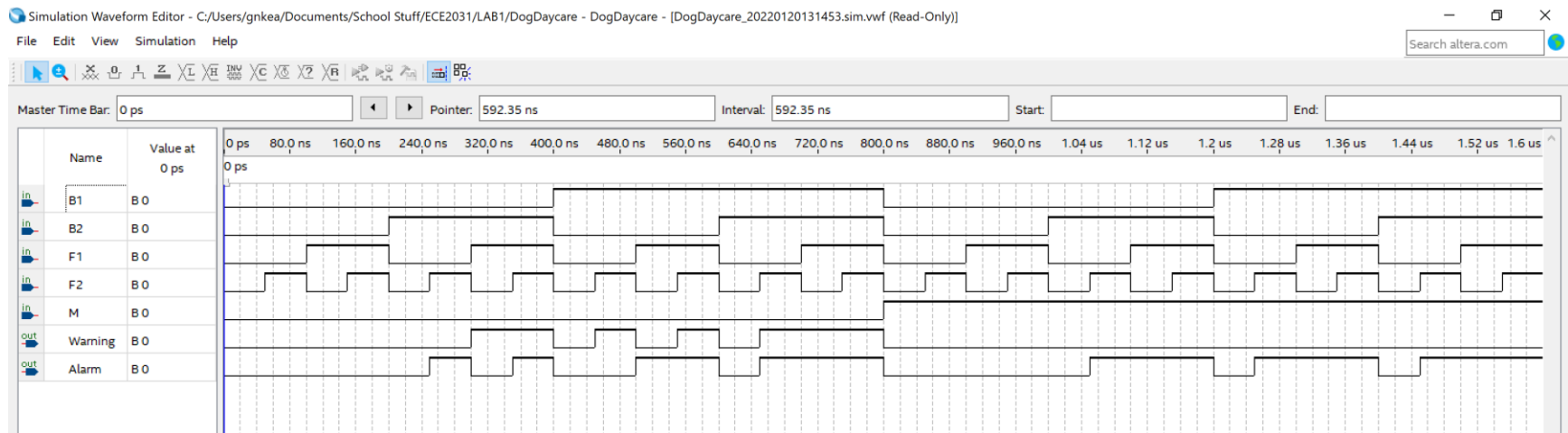


Figure 3. Functional simulation waveform implementing the dog alarm/warning system for all possible input combinations to confirm the accuracy of the circuit.

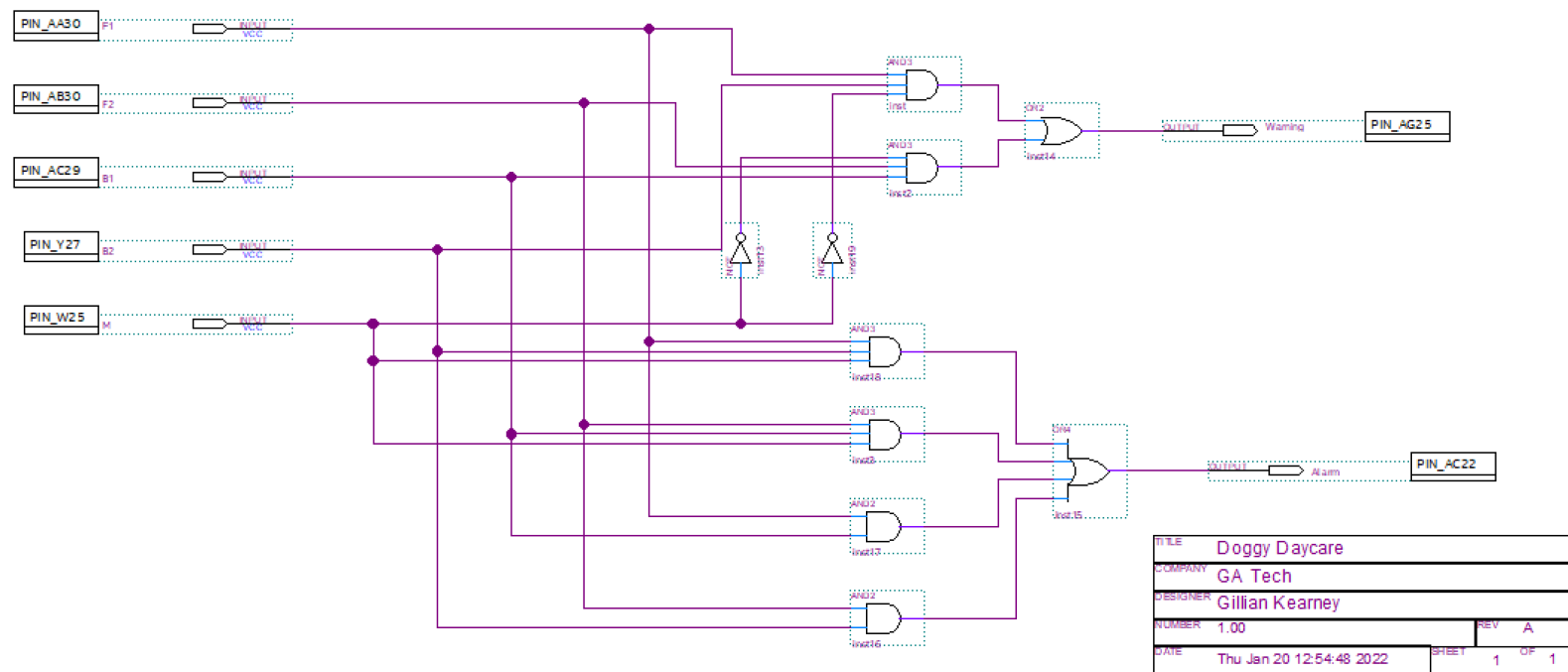


Figure 4. Circuit implementing the dog/alarm logic (Alarm = $F1 \cdot B1 + F2 \cdot B2 + F2 \cdot B2 \cdot M + F2 \cdot B1 \cdot M$ Warning = $F1 \cdot B2 \cdot /M + F2 \cdot B1 \cdot /M$) with specified pin locations for both inputs and outputs.