

Gillian Kearney

Lab Report 4

ECE 2031 L09

17 February 2022


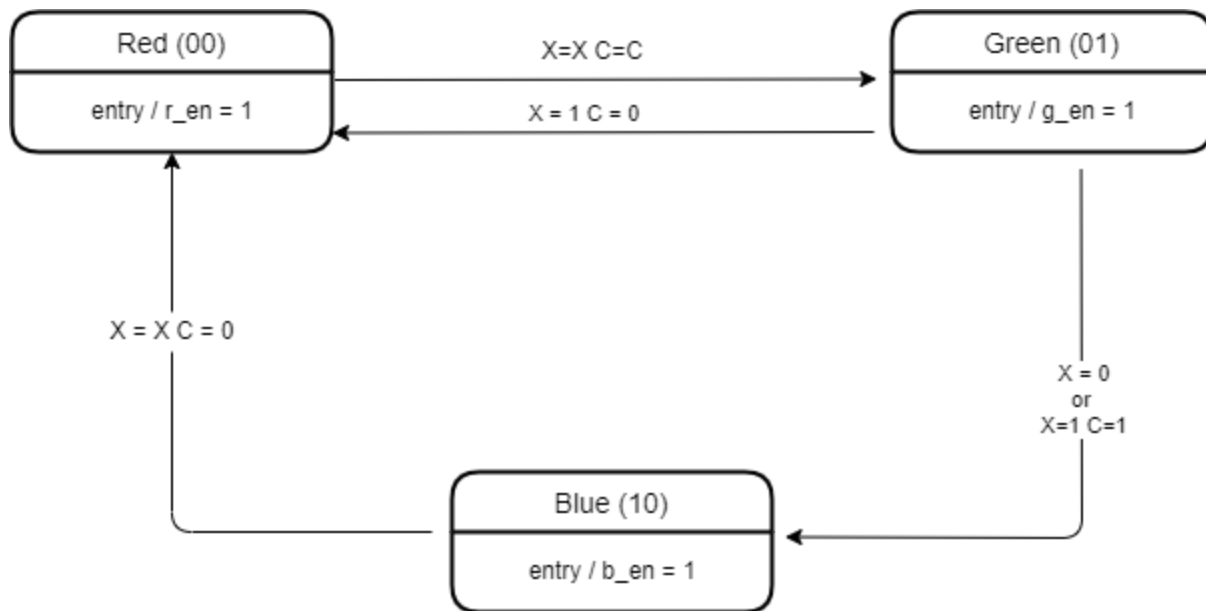


Figure 1. The state diagram of a finite state machine that rotates between Red, Green and Blue states. Each state shows what occurs on entry and the requirements to move to the succeeding state.

Current State	Q1	Q0	xmas	cool	Next State	Q1+	Q0+	r_en	g_en	b_en
Red	0	0	0	0	Green	0	1	1	0	0
Red	0	0	0	1	Green	0	1	1	0	0
Red	0	0	1	0	Green	0	1	1	0	0
Red	0	0	1	1	Green	0	1	1	0	0
Green	0	1	0	0	Blue	0	1	0	1	0
Green	0	1	0	1	Blue	0	1	0	1	0
Green	0	1	1	0	Red	0	0	0	1	0
Green	0	1	1	1	Blue	0	1	0	1	0
Blue	1	0	0	0	Red	0	0	0	0	1
Blue	1	0	0	1	Blue	0	1	0	0	1
Blue	1	0	1	0	Red	0	0	0	1	1
Blue	1	0	1	1	Blue	0	1	0	1	1

Figure 2. The transition table of a finite state machine that rotates through states Red, Green, and Blue. The table shows all possible combinations of current state and inputs excluding the unused state (11)

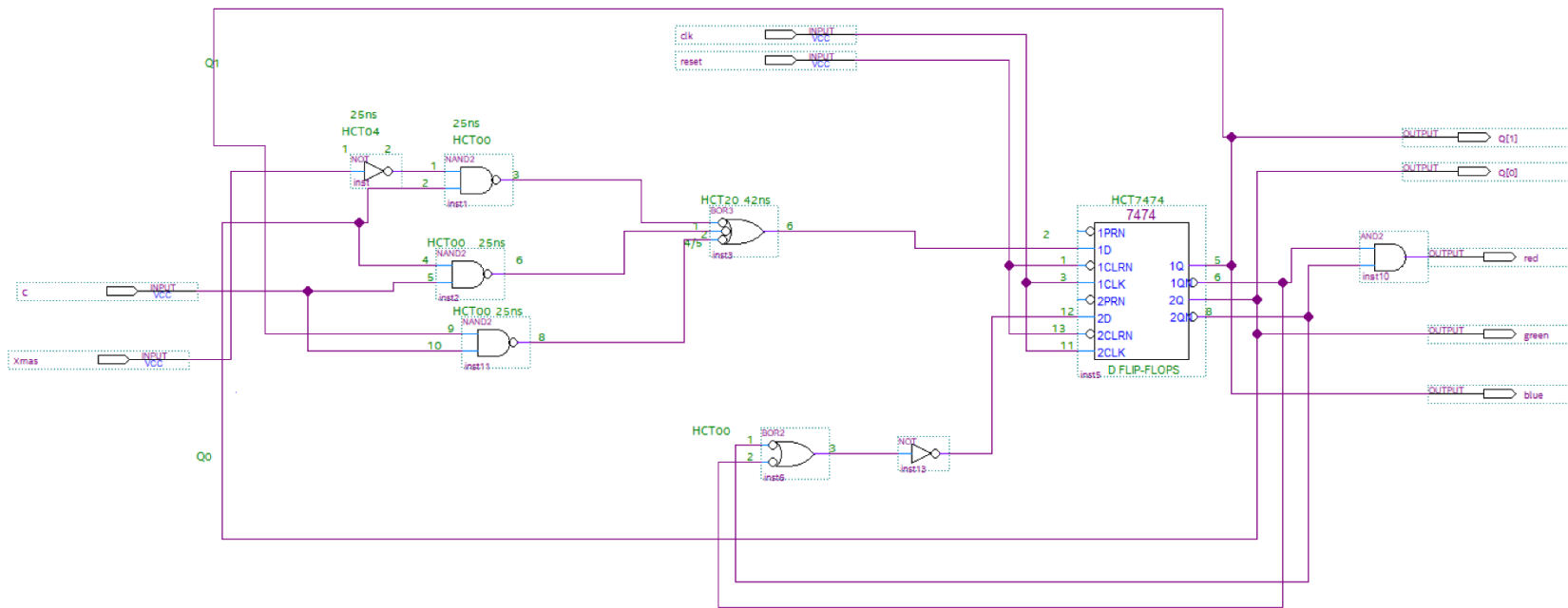

TITLE	Ligt State Machine		
COMPANY	GA Tech		
DESIGNER	Gillian Kearney		
NUMBER	1.00	REV	A
DATE	Thu Feb 10 18:32:45 2022	SHEET	1 OF 1

Figure 3. Circuit Schematic implementing a finite state machine. Outputs red, green, and blue activate in a cycle continuously unless interrupted by an input of c or xmas in which blue stays active or red and green cycle respectively.

 


Figure 4. Functional simulation waveform of Red, Green, Blue finite state machine with 4 inputs and 4 outputs. The input vector covers all possible input states to prove the correctness of the circuit.


 


Figure 5. The circuit implementation of a finite state machine where the next state is monitored by led lights found on the bottom right and top middle of the circuit.

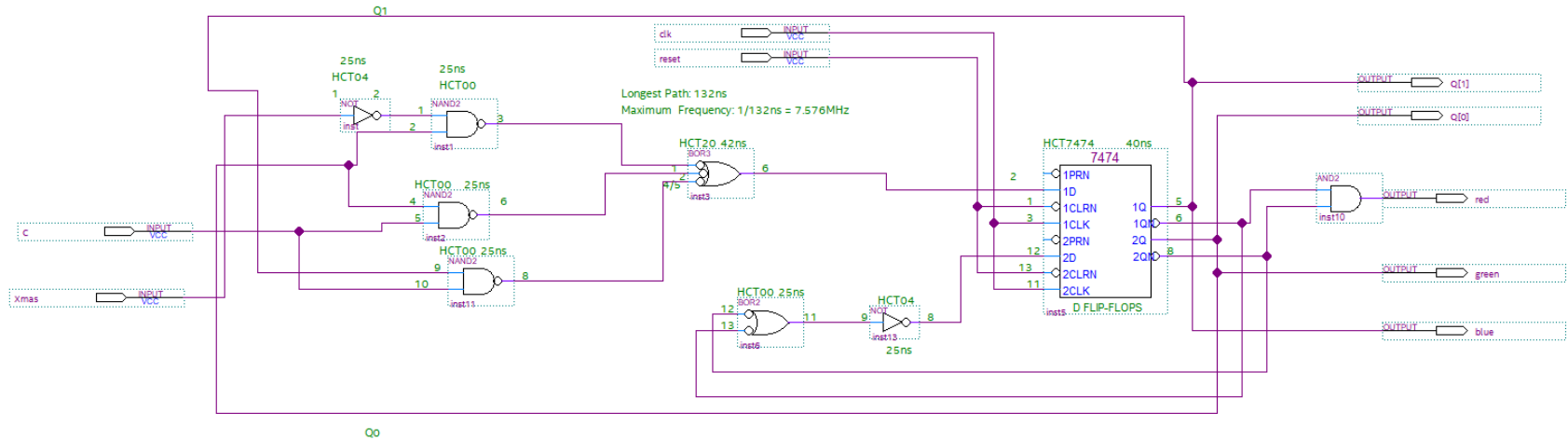

TITLE	Light State Machine		
COMPANY	GA Tech		
DESIGNER	Gillian Kearney		
NUMBER	1.00	REV	A
DATE	Thu Feb 17 00:44:59 2022	SHEET	1 OF 1

Figure 6. Circuit Schematic implementing a finite state machine. It shows each gate's worst case propagation delay and the circuit's worst possible delay of 132ns which runs through the upper path, through an inverter, 2 nand gates and a D flip-flop. The calculated maximum frequency was found to be 7.576MHz.